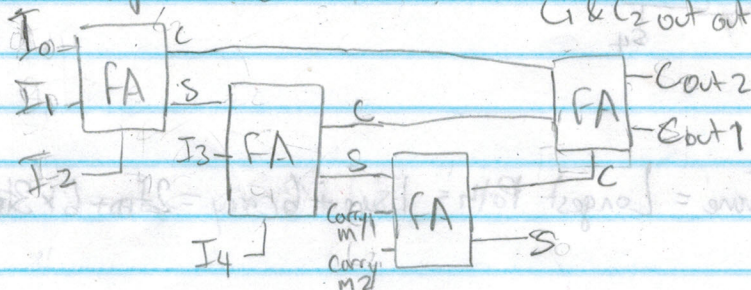


Collaborators:


Hanyu Yun, Kyle Wong.

Online Resources:

1. Five Input Adder

(Assumes C_1 & C_2 are one's place)
 C_1 & C_2 out out ones and two's place


$$\text{Propagation Delay} = 4 \times \text{FA} = 4 \times 3 \text{tpd} = 12 \text{tpd}$$

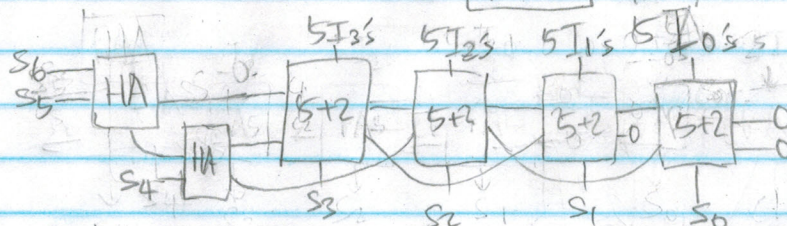1.2 The sum should have $4+3=7$ bits.

$$\text{Propagation Delay} = 2\text{HA} + 4 \times \text{FA} = 6 \text{tpd} + 4 \times 12 \text{tpd} = 54 \text{tpd}$$

Full Adders: $2 + 4 \times 4 = 18$ full adders total

Other method:

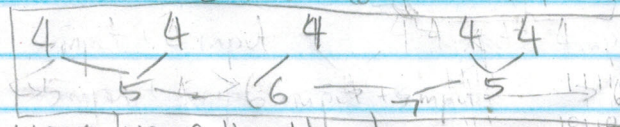Requires $4+4+5+6=19$ full addersTime is longest path: $4 \times 3 \text{tpd} + 5 \times 3 \text{tpd} + 6 \times 3 \text{tpd} = 45 \text{tpd}$